




Introduction

Electrical & Electronic Circuits and Elements

Embedded Systems & Embedded Programming

Fundamentals of Electric Circuits (Inductor)


- ❖ Is a passive element that **stores energy** in its **magnetic field**
- ❖ Is used in power supplies, transformers, radios, radars, electric motors and etc.
- ❖ Any conductor of electric current has inductive properties and may be regarded as an inductor
- ❖ To enhance the inductive effect, a practical inductor consists of a **coil of conducting wire**
- ❖ **Inductance** is the property that an inductor shows opposition to the change of current
 - Measured in henrys (**H**)
 - Depends on the physical dimension and construction of the inductor
 - Represented by **L**

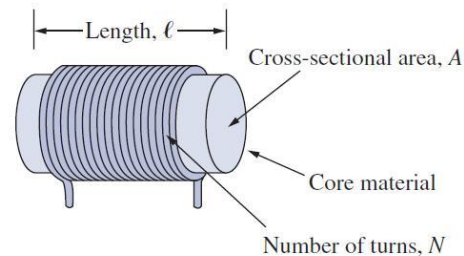

Typical form of an inductor.

$$L = \frac{N^2 \mu A}{\ell}$$

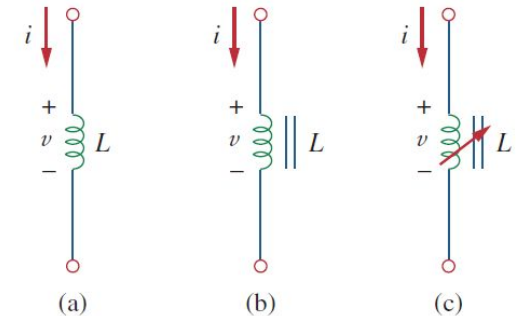μ is the permeability of the core
 μ for air is 1.257×10^{-6} H/m




Circuit symbols for inductors: (a) air-core, (b) iron-core, (c) variable iron-core.

Fundamentals of Electric Circuits (Inductor)

- ❖ The voltage across an inductor is directly proportional to the time rate of change of the current
- ❖ An inductor acts like a short circuit to dc current
 - The voltage across an inductor is zero when the current is constant
- ❖ The current through an inductor cannot change instantaneously
 - Discontinuous change in the current requires an infinite voltage



[Inductors and Inductance](#)

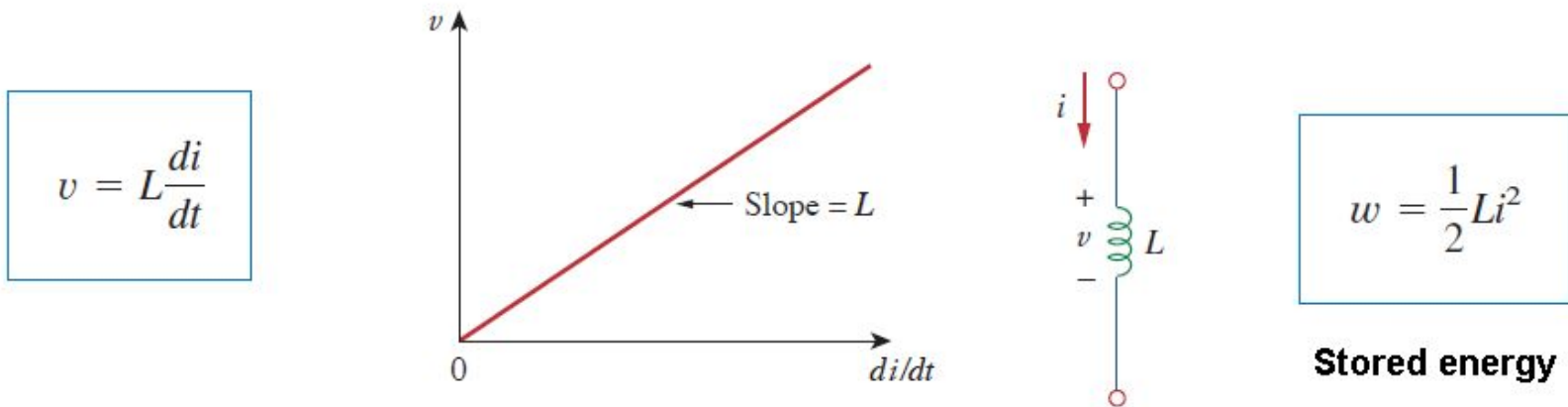


Stored energy



Voltage-current relationship of an inductor.

Fundamentals of Electric Circuits (Inductor)

- ❖ An ideal inductor does not dissipate energy
 - It takes power from the circuit when storing energy
 - Delivers power to the circuit when returning previously stored energy
- ❖ A practical inductor has significant:
 - Resistance because of the
 - Conducting material
 - Capacitance because of the
 - Capacitive coupling between the conducting coils
- ❖ Impedance of an inductor is sL where
 - s is the complex frequency of the source signal
 - s for a **DC** signal is **0** and for a **sinusoidal AC** signal is $j\omega$
 - $\omega = 2\pi f$ where f is the frequency of the signal

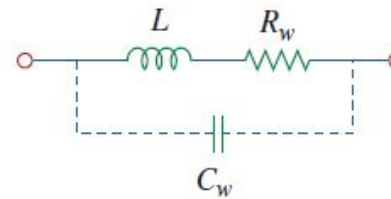


Circuit model for a practical inductor.

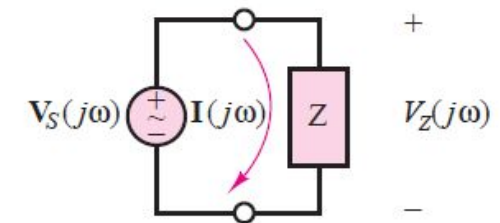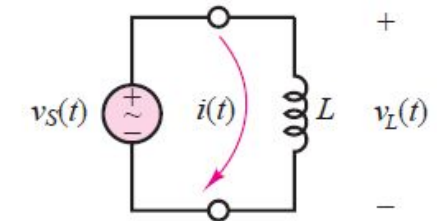

Fundamentals of Electric Circuits (Inductor)

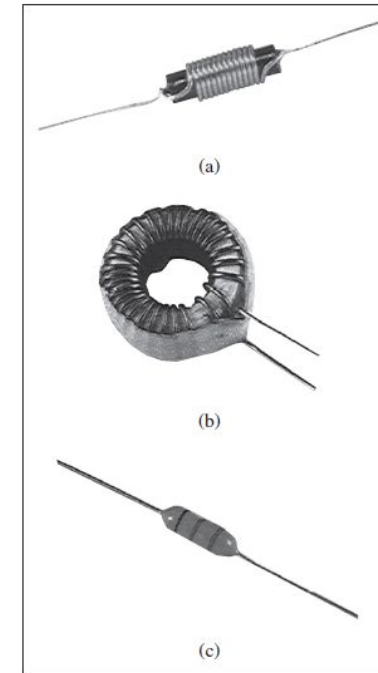- ❖ Measured by
 - [Online Calculator](#)
 - Inductance meter
 - By [text or color marking](#) on the inductor
- ❖ Some useful links
 - [The Inductor](#)
 - [Inductance of a Coil](#)
 - [Mutual Inductance](#)
 - [Inductors in Series](#)
 - [Inductors in Parallel](#)




Various types of inductors: (a) solenoidal wound inductor, (b) toroidal inductor, (c) chip inductor.





Fundamentals of Electric Circuits (Inductor)

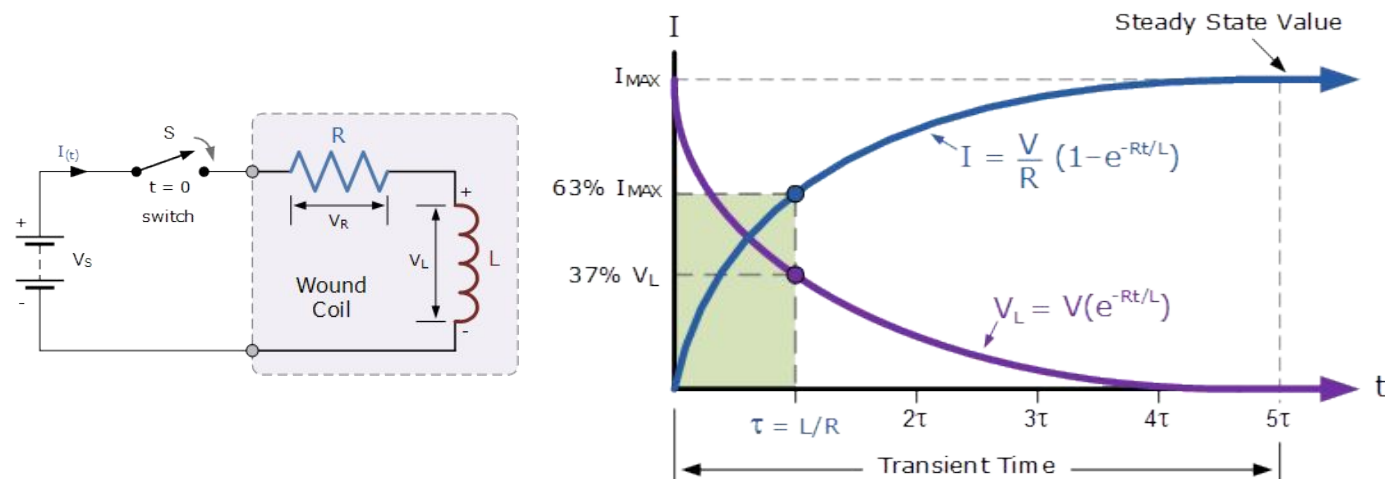- ❖ Store and release energy
 - [LR Series Circuit](#)
- ❖ AC, puls and etc. responses
- ❖ Applications
 - Filters
 - [Transformers](#)






$$\frac{N_P}{N_S} = \frac{V_P}{V_S} = n = \text{Turns Ratio}$$
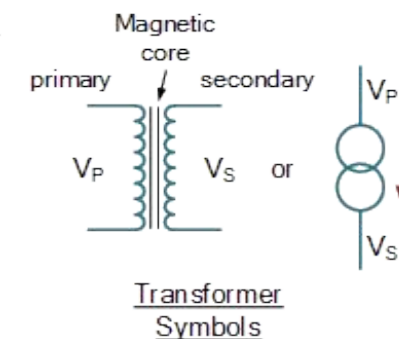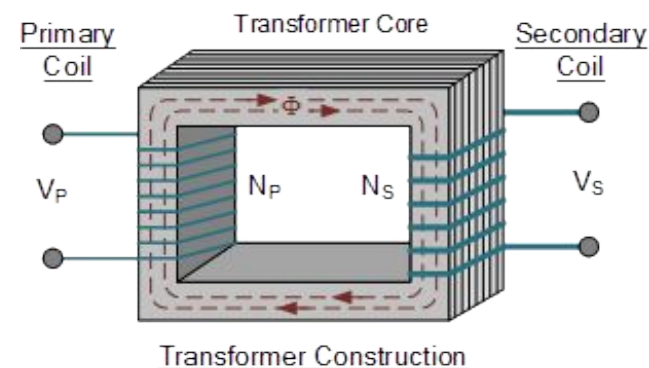
$$\text{Power}_{\text{Primary}} = \text{Power}_{\text{Secondary}}$$



Fundamentals of Electric Circuits (Electromagnetism)

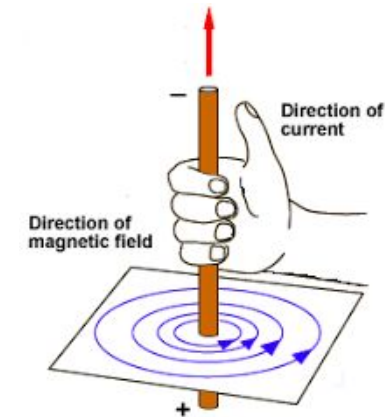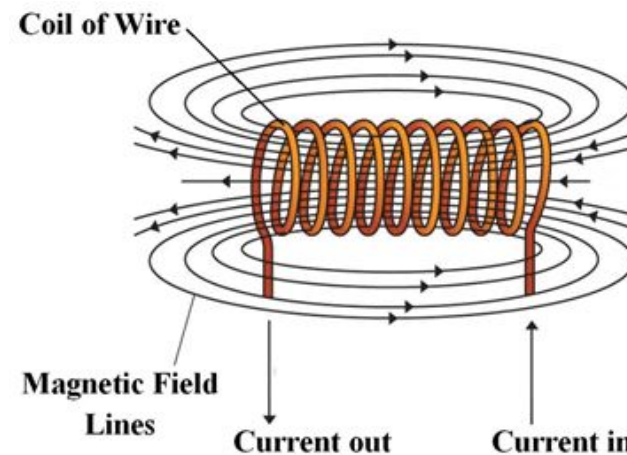
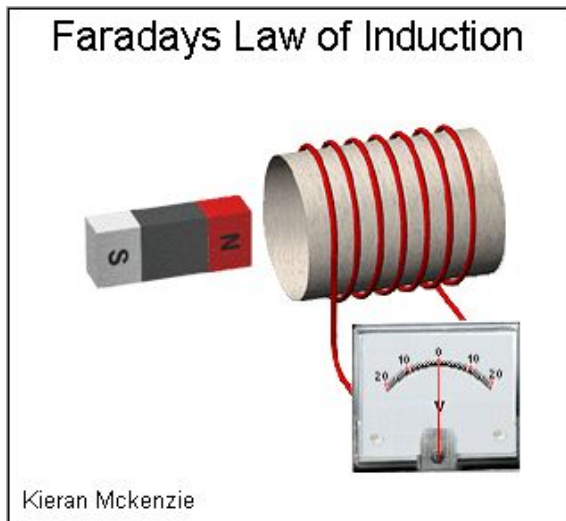
- ❖ A moving electric charge (**current**) generates a **magnetic field**
- ❖ A **magnetic field** induces electric charge movement (**current**)
- ❖ Electricity and magnetism are two related phenomena produced by the **electromagnetic** force
- ❖ In an [electromagnetic wave](#), the electric and magnetic fields are perpendicular to each other



Fundamentals of Electric Circuits (Transmission Line)

- ❖ To deliver power, connection of two wires between the source and the load is required
- ❖ At low frequencies, power is delivered to the load in electric fields
- ❖ At higher frequencies, power is delivered in electric and magnetic fields
- ❖ Transmission line is a material structure that transfers energy in form of electromagnetic field
- ❖ If the impedance of the load and the transmission line are not matched
 - Some part of the power will be reflected to the source
 - The reflection coefficient at the load is

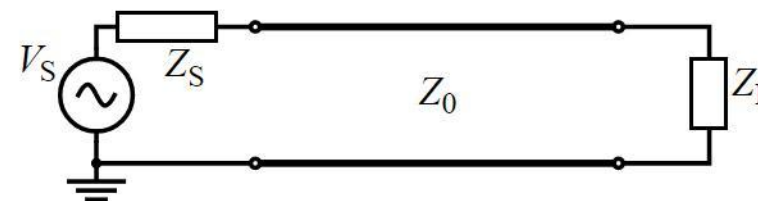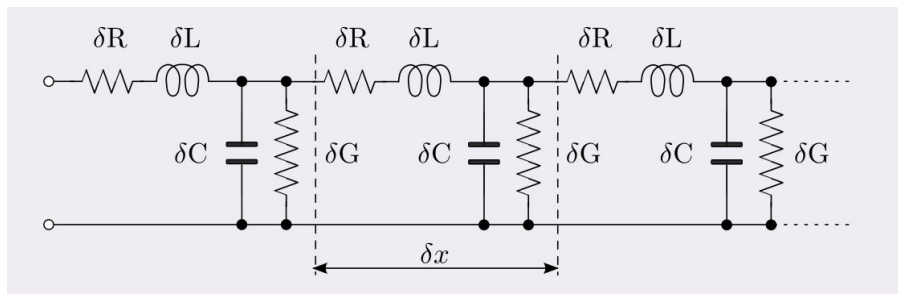
$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$



[Transmission Lines - Signal Transmission and Reflection](#)


Fundamentals of Electric Circuits (Ground Loops)

- ❖ Ground loop exists when an electrical system is connected through more than one path to the ground
- ❖ Ideally, all grounded points of an electrical system should be at the same potential
- ❖ The ground loop forms a large loop antenna that picks up interference currents easily
- ❖ The larger the loop the more interference (EMI)
- ❖ Result: The ground is no longer stable
- ❖ [Ground Loops: Avoid Them!](#)
- ❖ [Grounding and Shielding of electric circuits](#)
- ❖ [Galvanic Isolation: Purpose and Methodologies](#)

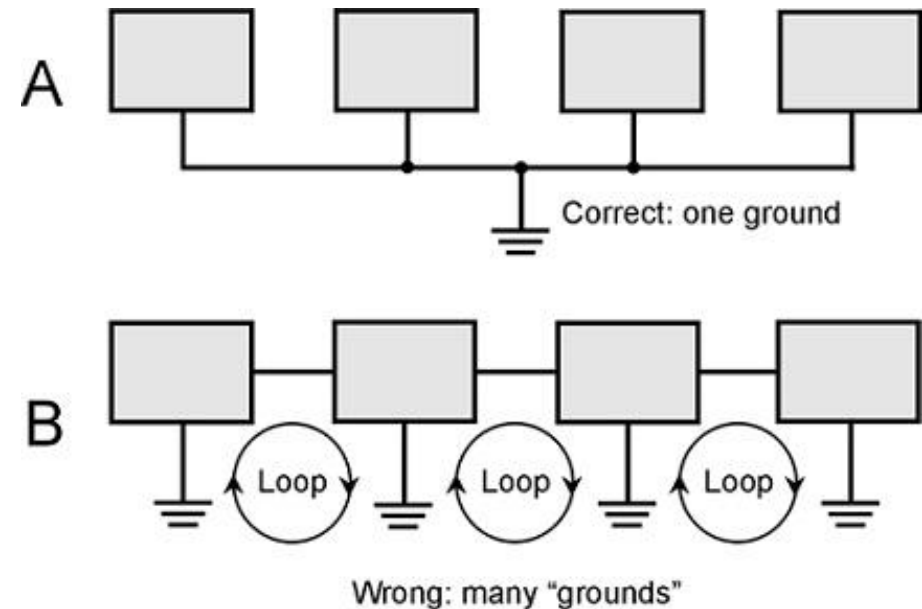

Fundamentals of Electric Circuits (Crosstalk)

- ❖ Electromagnetic (EM) Crosstalk is an unwanted interference
- ❖ It is caused by the electric and magnetic fields of one or more signals affecting another signal
- ❖ Crosstalk occurs via two mechanisms
 - Capacitive crosstalk caused by the electrical field
 - Inductive crosstalk caused by the magnetic field
- ❖ Some solutions
 - Shielding
 - Increase the distance between lines
 - Using twisted pair wires
- ❖ [Crosstalk \(electronics\)](#)
- ❖ [CrossTalk](#)

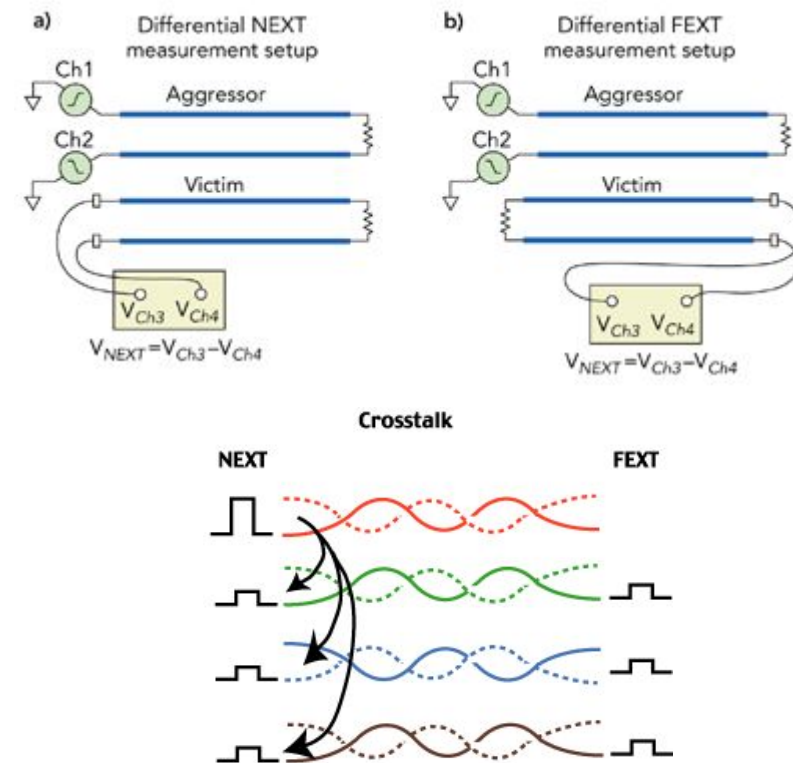

Fundamentals of Electric Circuits

❖ References

- Fundamentals of Electric Circuits, 5th Edition, Charles K. Alexander and Matthew N.O. Sadiku, ISBN 978-0-07-338057-5
- Fundamentals of Electrical Engineering, First Edition, Giorgio Rizzoni, ISBN 978-0-07-338037-7
- ***Some of the images have been copied from these two books***

❖ Some useful links

- [Electronic Basics #12: Coils / Inductors \(Part 1\)](#)
- [Inductance basics](#)
- [Do Volts or Amps Kill You? Voltage, Current and Resistance](#)
- [How does an Antenna work? | ICT #4](#)
- [Electromagnetic interferences](#)
- [What is Hall Effect and How Hall Effect Sensors Work](#)

The SI prefixes.

Multiplier	Prefix	Symbol
10^{18}	exa	E
10^{15}	peta	P
10^{12}	tera	T
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10^2	hecto	h
10	deka	da
10^{-1}	deci	d
10^{-2}	centi	c
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p
10^{-15}	femto	f
10^{-18}	atto	a