



Introduction

Electrical & Electronic Circuits and Elements

Embedded Systems & Embedded Programming

Fundamentals of Electronic Circuits (Field Effect Transistors)

❖ Field Effect Transistor (**FET**)

- Has three terminals (**Source**, **Gate** and **Drain**)
- Can be used as switch, amplifier, resistor, capacitor and etc.
- Is high efficiency and robust and can be used in most applications to replace **BJTs**
- Is a unipolar semiconductor device (charge carriers are electrons **or** holes)
- Unlike **Bipolar Junction Transistor**, it is controlled by an electric field (**Gate Voltage**)
- Two basic classifications: the **N-channel FET** and the **P-channel FET**
- Has a very high input impedance (more than $10^9\Omega$)
 - Very sensitive to input voltage signal and can be easily damaged by static electricity
 - Lower power consumption and smaller than an equivalent BJT transistor
 - Very low gate leakage current (less than 10^{-9}A)
- Types of FETs: **JFET**, **MOSFET**, MESFET, FinFET and etc.



[Field Effect Transistors](#)

Fundamentals of Electronic Circuits (Field Effect Transistors)

❖ Field Effect Transistor (**FET**)

- It has a high power gain and It can deliver more power than BJT
- It is less noisy and has a higher frequency response in compare with BJT
- Has a very low "ON" resistance and have a high "OFF" resistance
- It can dissipate large amounts of power while switching
- It provides more thermal stability
- Applications
 - FETs are widely used in analog and digital circuits
 - Power converters and suppliers, RF power amplifiers and etc.
 - Integrated circuits like processors such as the **CMOS** range of digital logic chips
 - Sensors; like pressure and image sensors
 - Volatile and non-volatile memories




 [Field Effect Transistor Types & Technology](#)

Fundamentals of Electronic Circuits (JFET)

❖ Junction Field Effect Transistors (JFETs)



- Two types: P-channel and N-channel
- They are depletion type transistors only
- They typically offer about $10^9 \Omega$ of input impedance
- The gate-channel junctions are reverse-biased
 - Otherwise whole the current from source will flow to the gate and the device gets damaged
- Can operate in four regions
 - Cut-off or pinch-off region
 - Ohmic or triode region
 - Saturation or active region
 - Breakdown region

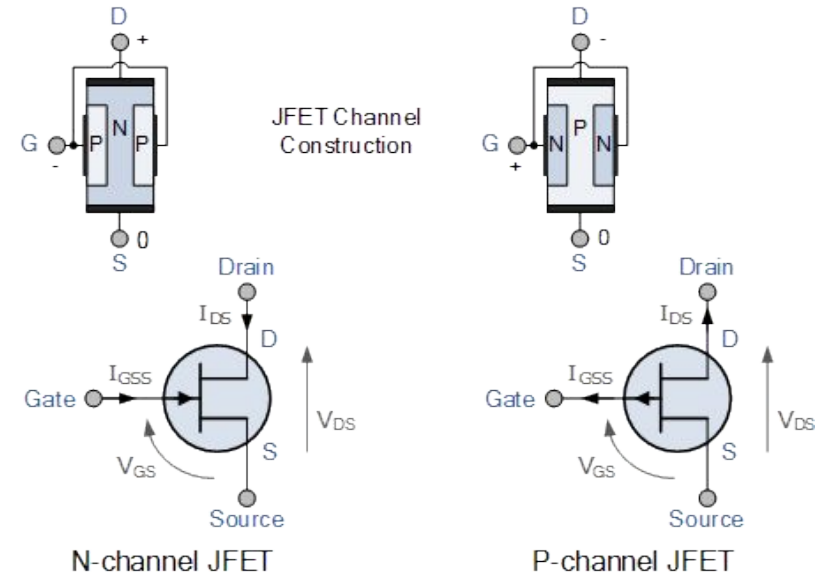

 [Junction Field Effect Transistor](#)

Fundamentals of Electronic Circuits (JFET)


- ❖ JFETs are specified in term of I_{DSS} and V_P ; i.e $V_{GS(off)}$
 - Pinch-off voltage (V_P) is the voltage at which the channel is closed
 - Drain to source saturation current (I_{DSS}) when $V_{GS} = 0$
 - V_P for N-channel is negative and for P-channel is positive
- ❖ Biasing of an N-channel JFET
 - With $V_{GS} = 0$ and small V_{DS}
 - Maximum saturation current (I_{DSS}) will flow through the channel from the drain to the source restricted only by the small depletion region around the junctions and $R_{DS(on)}$ is about 0.05Ω
 - By decreasing the V_{GS} , the width of the depletion region is increased which in turn reduces the conduction of the channel
 - When the $V_{GS} \leq V_P$, the channel will be closed and no more current flows between the drain and the source ($I_D = 0$)

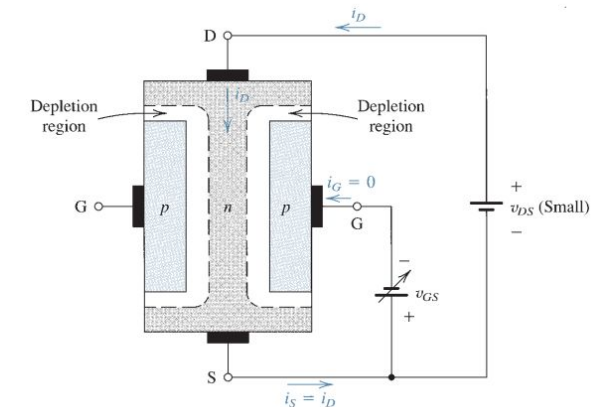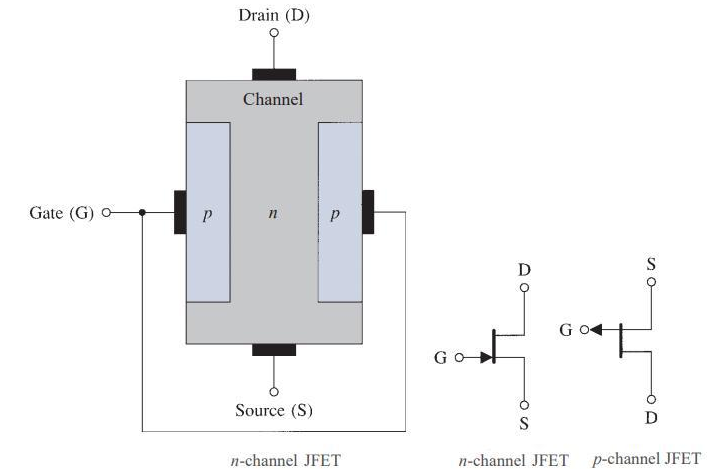

Fundamentals of Electronic Circuits (JFET)

❖ Biasing of an N-channel JFET

- With $V_P \leq V_{GS} \leq 0$ and increasing the V_{DS} from Zero
 - The most-depleted portion of the depletion region is in between the gate and the drain, while the least-depleted area is between the gate and the source
 - The depleted portion of the depletion region between gate and drain increases and therefore the conduction of the channel reduces
 - When $V_{DS} \geq V_{GS} - V_P$, then the channel gets saturated and
 - The drain current I_D no longer increases with increasing of V_{DS}
 - The drain current I_D remains fairly constant
 - If V_{DS} is continuously increased, the junctions are broken and the JFET may be destroyed


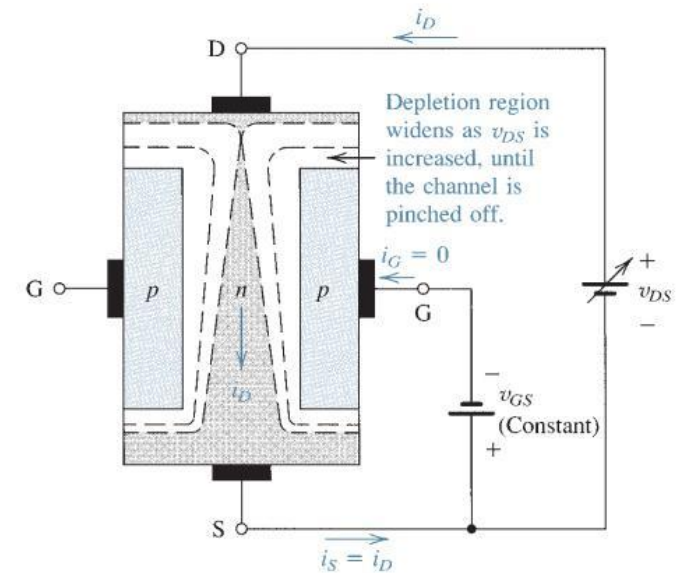


[!\[\]\(d3fb9f94af8b26d1c844efa9a98805b0_img.jpg\) Characteristics of JFETS](#)

Fundamentals of Electronic Circuits (N-channel JFET)

❖ Four different regions of operation for a JFET

- Cut-off ($V_{GS} \leq V_P$)
 - Where V_{GS} is sufficient to cause the JFET to act as an open circuit as the channel resistance is at maximum ($I_D = 0$)
- Ohmic or triode ($V_P < V_{GS} \leq 0$ and $V_{DS} \leq V_{GS} - V_P$)
 - The depletion layer of the channel is small and the JFET acts like a voltage controlled resistor
- Saturation or active ($V_P < V_{GS} \leq 0$ and $V_{DS} > V_{GS} - V_P$)
 - It becomes a good conductor controlled by V_{GS}
 - V_{DS} has little or no effect and the device is used as an amplifier
- Breakdown
 - V_{DS} is high enough to causes the channel to break down and pass uncontrolled maximum current

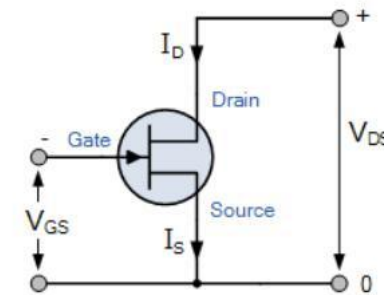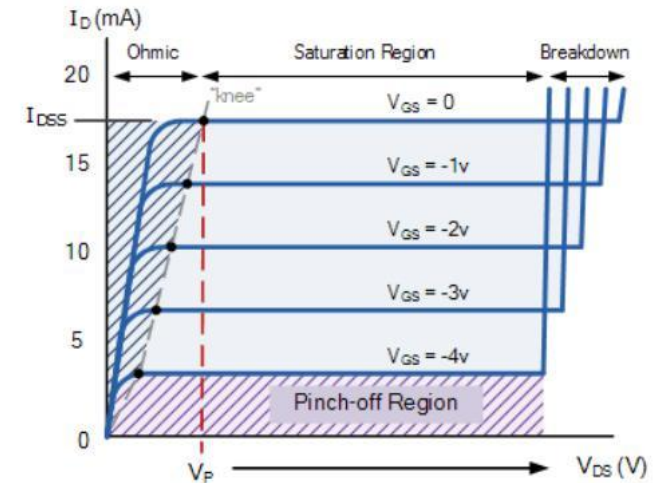

KVL: $V_{DS} = V_{DG} + V_{GS}$, KCL: $I_G = 0$, $I_D = I_S$

Fundamentals of Electronic Circuits (N-channel JFET)

- ❖ The drain-source current in ohmic region is

$$i_D = I_{DSS} \left[2 \left(1 - \frac{V_{GS}}{V_P} \right) \left(\frac{V_{DS}}{-V_P} \right) - \left(\frac{V_{DS}}{V_P} \right)^2 \right]$$


- ❖ The drain-source current in saturation region is

$$i_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

- ❖ Transconductance gain of the JFET in active mode is

$$g_m = \left(\frac{2I_{DSS}}{|V_P|} \right) \left(1 - \frac{V_{GS}}{V_P} \right)$$

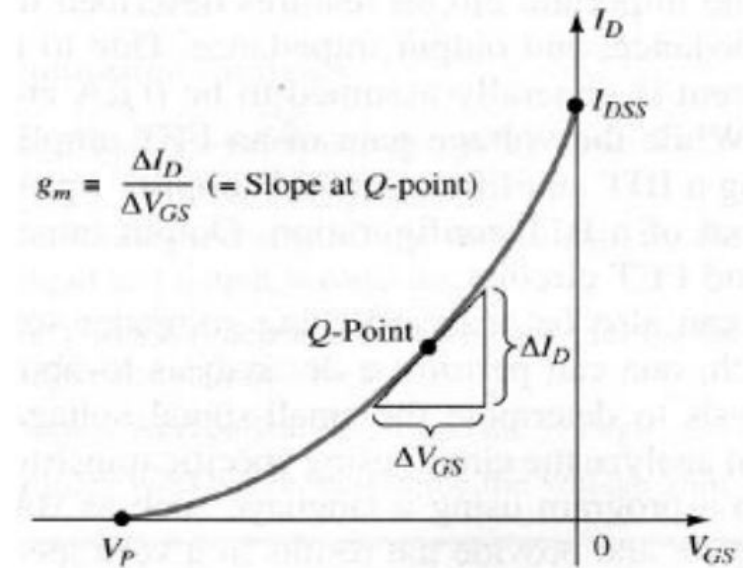- Where g_m is the ratio of change in drain current, ΔI_D , to the change in gate-source voltage, ΔV_{GS} .
- Its unit is $1/\Omega$ (mho or Siemens)



[How FETs Function - The Learning Circuit](#)

Fundamentals of Electronic Circuits (MOSFET)

❖ Metal Oxide Semiconductor Field Effect Transistor (MOSFET)

- The gate is physically insulated from the channel by an oxide layer (SiO_2)
- Voltage applied to the gate controls the conductivity of the channel
 - As a result of the electric field induced capacitively across the insulating dielectric layer






- Both N-channel (NMOS) and P-channel (PMOS) variants are available
- Both enhancement and depletion types are available
- Typically offers more than $10^{14} \Omega$ of input impedance
- Is the most manufactured device in history

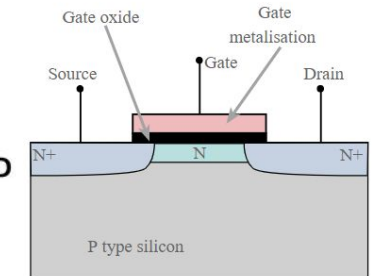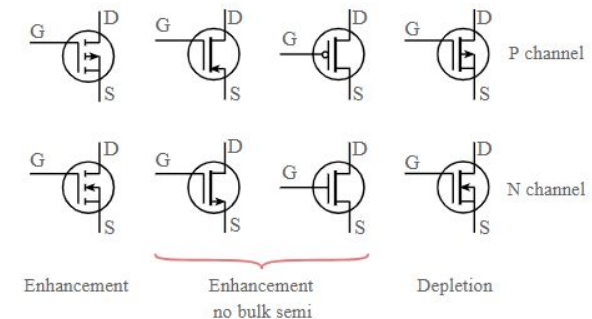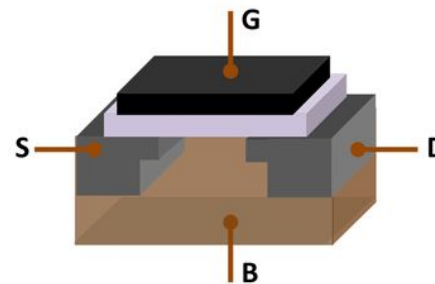
- 1.3×10^{22} MOSFETs between 1960 and 2018

➤ Three terminals

- Gate, Drain, Source
- Bulk/Body is connected to source or has no effect (in no bulk E-MOSFET)



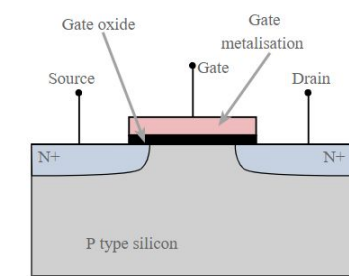N channel depletion mode MOSFET structure



N channel enhancement mode MOSFET structure

Fundamentals of Electronic Circuits (MOSFET)

❖ Depletion MOSFET

- it consists of a channel diffused between the drain to source terminal
- It requires the Gate-Source voltage, (V_{GS}) to switch the device “OFF”
- It is equivalent to a “Normally Closed” switch
- Its behaviour is almost like a JFET but because of the insulated gate



[Depletion Type MOSFET: What is it?](#)

- it is possible to bias its gate in either polarity, positive or negative
- For example in a N-channel MOSFET



- More $+V_{GS}$ means more current
- While more $-V_{GS}$ means less current

- Operate within three different regions

- Cut-off, Linear (Ohmic) and Saturation

- Is less common than the enhancement mode types

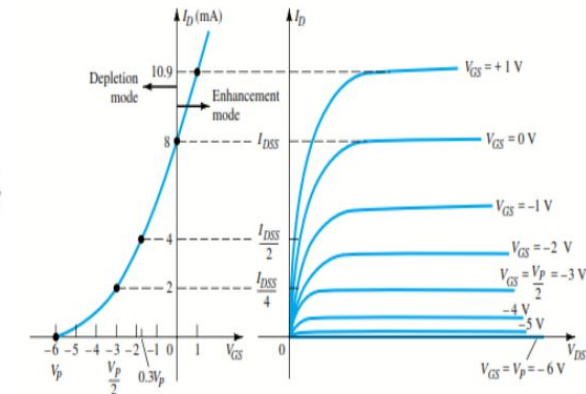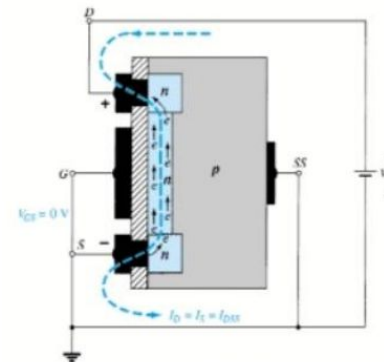- Like a JFET, it is specified in term of I_{DSS} and V_P




$$i_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

Fundamentals of Electronic Circuits (MOSFET)

❖ Enhancement MOSFET (eMOSFET)


- The conducting channel is lightly doped or even undoped
- The device is normally “OFF” when V_{GS} is 0V
- It requires a Gate-Source voltage to switch the device “ON”
- It is equivalent to a “Normally Open” switch
- For an n-channel eMOSFET
 - + V_{GS} turns it “ON”, while a zero or - V_{GS} turns it “OFF”
 - Increasing the + V_{GS} will decrease the channel resistance
- A drain current will only flow when V_{GS} greater than the threshold voltage (V_{TH})
- It is an excellent electronics switch due to its
 - Infinitely high input impedance
 - Low “ON” and extremely high “OFF” output impedances
- eMOSFETs are used in ICs to produce CMOS type Logic Gates and power switching circuits

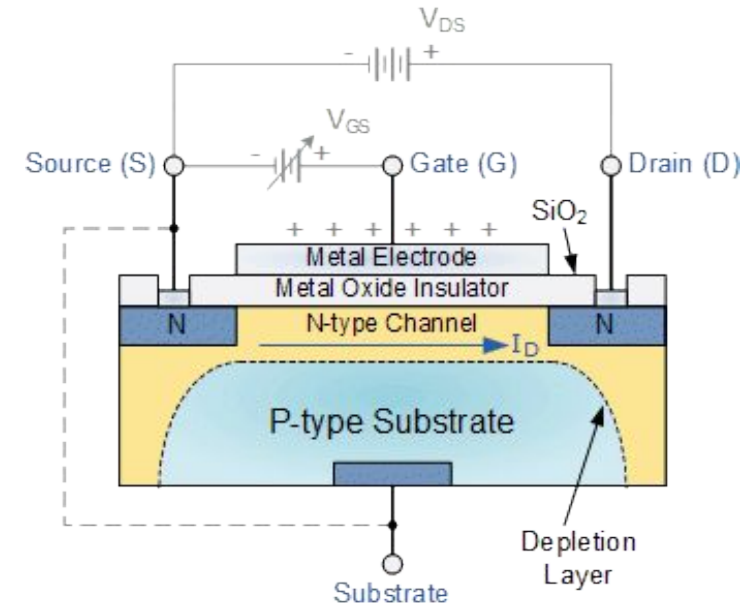

[MOSFET Transistor Basics & Working Principle](#)

Fundamentals of Electronic Circuits (MOSFET)

- ❖ An eMOSFET is specified in term of (V_{th}) and K_n
 - V_{th} (threshold) is the minimum required V_{GS} to make the device conducting
 - K_n is the conductance coefficient and it can be calculated from
 - $I_{D(on)}$ and $V_{GS(on)}$ form its datasheet
- ❖ eMOSFET operation modes
 - Cut-off Region ($V_{GS} \leq V_{th}$):
 - It is “fully-OFF” thus, $I_D = 0$
 - It acts like an open switch regardless of the value of V_{DS}
 - Ohmic Region ($V_{GS} > V_{th}$ and $V_{DS} \leq V_{GS} - V_{th}$):
 - It acts like a voltage-controlled resistance
 - Saturation Region ($V_{GS} > V_{th}$ and $V_{DS} > V_{GS} - V_{th}$):
 - It is “fully-ON” and the drain current is maximum
 - It acts like a closed switch

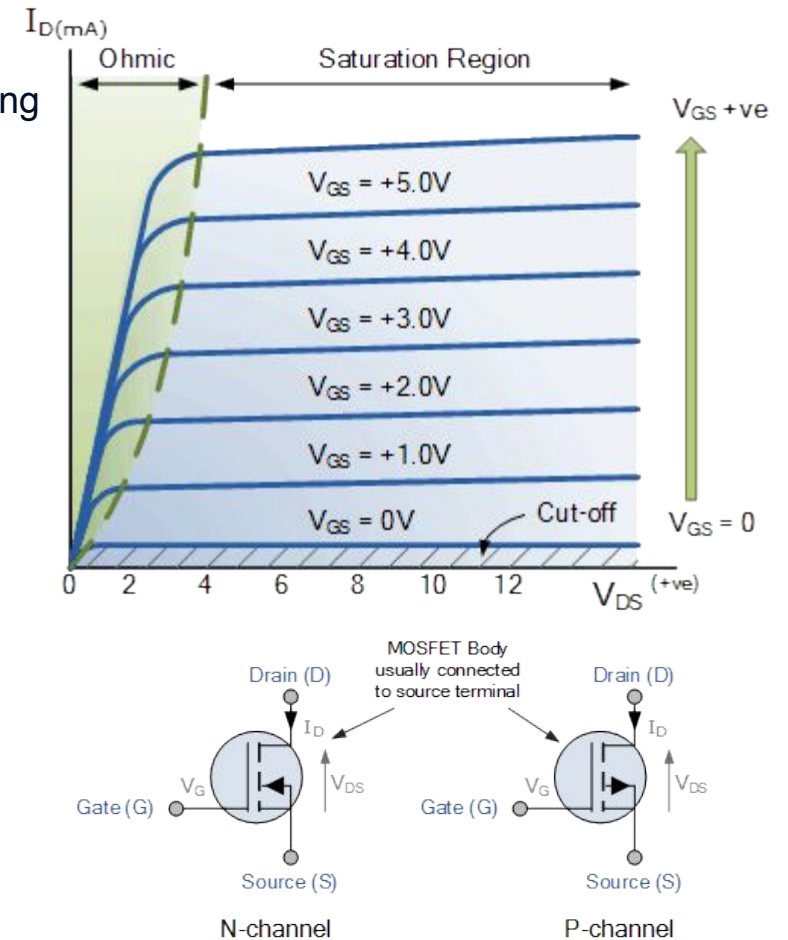

Fundamentals of Electronic Circuits (MOSFET)


- ❖ The conductance coefficient is $k_n = \mu_n C_{ox} \frac{W}{L}$
 - μ_n is the charge-carrier effective mobility, C_{ox} is the gate oxide capacitance per unit area
 - W is the gate width and L is the gate length
- ❖ The drain current in ohmic mode is
 - $I_D = K_n(V_{GS} - V_{th} - 0.5V_{DS})V_{DS}$
- ❖ The drain current in saturation mode is
 - $I_D = 0.5 \times K_n(V_{GS} - V_{th})^2$
- ❖ The gain of an eMOSFET in saturation mode is
 - $g_m = 2 \times K_n \times (V_{GS} - V_{th})$



[MOSFETs and How to Use Them | AddOhms](#)



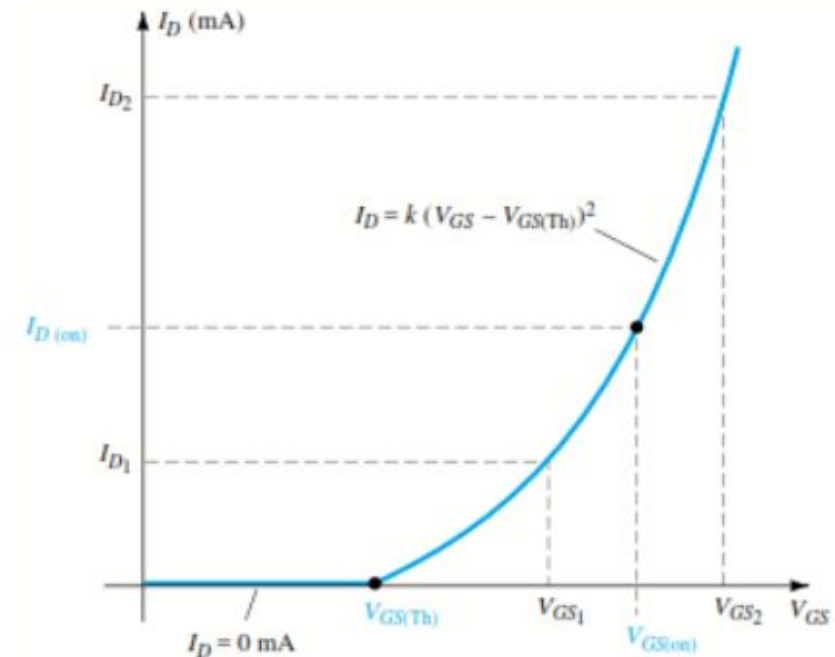[Power Electronics - MOSFET Power Losses](#)




Fundamentals of Electronic Circuits (MOSFET)

❖ MOSFET as a switch

➤ OFF State

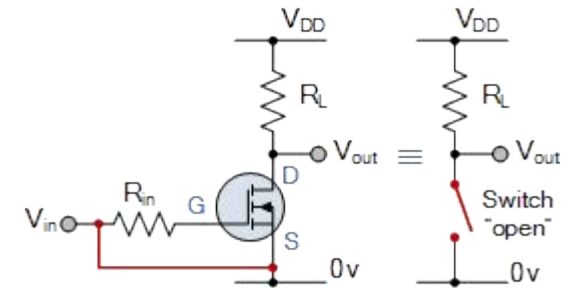
- $V_{GS} = 0V$ and $V_{GS} < V_{TH}$
- MOSFET is “OFF” and $I_D = 0A$
- MOSFET operates as an “open switch”
- $V_{OUT} = V_{DS} = V_{DD} == \text{HIGH}$



The MOSFET is in the cut-off mode


➤ ON State

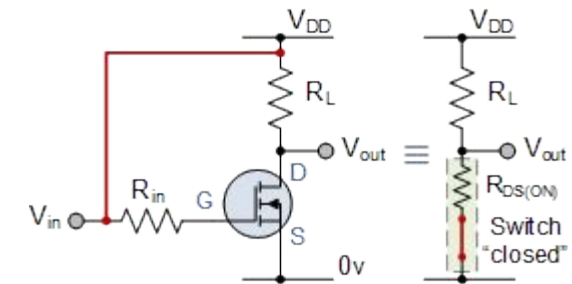
- $V_{GS} = V_{DD}$ and $V_{GS} > V_{TH}$
- MOSFET is “ON” and $I_D = V_{DD} / R_L$
- $V_{DS} = 0V$ (ideal saturation) and channel resistance $R_{DS(on)} < 0.1\Omega$
- MOSFET operates as a low resistance “closed switch”
- $V_{OUT} = V_{DS} \approx 0.2V$ due to $R_{DS(on)}$



The MOSFET is in saturation mode

Fundamentals of Electronic Circuits (MOSFET)

- ❖ Example: Calculate V_{GS} , V_{DS} and I_D
- ❖ Known values
 - $V_{GG} = 1.5V$, $V_{DD} = 7V$, $V_{th} = 1V$, $K_n = 1.2mA/V^2$ and $R_D = 7\text{ k}\Omega$
- ❖ Answer
 - $I_G = 0$, $V_{GS} = V_{GG} = V_G - V_S = 1.5V$
 - $V_{GS} > V_{th}$, we assume that the MOSFET is in saturation mode
 - $I_D = 150\text{ }\mu A$ and $V_{DS} = 5.95V$
 - $V_{DS} > V_{GS} - V_{th} \Rightarrow 5.95 > 1.5 - 1$  so the transistor is in the saturation mode

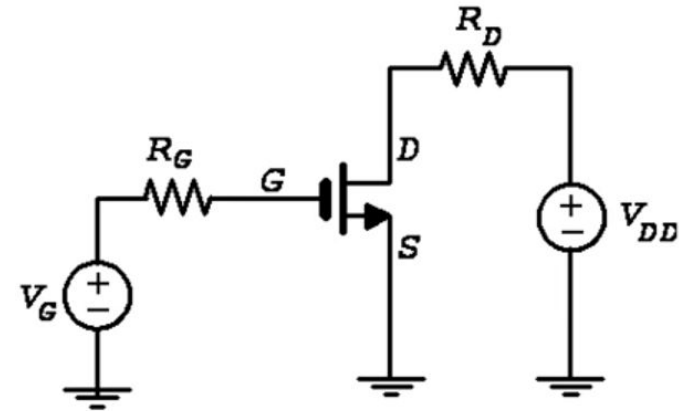

 [The MOSFET](#)

 [MOSFET as a Switch](#)


Fundamentals of Electronic Circuits (CMOS)

❖ CMOS (Complementary MOS)

- Is a type of MOSFET fabrication process
- Uses complementary and symmetrical pairs of NMOS and PMOS for logic function

❖ Features

- Dissipates low power
 - At 1 MHz and 50 pF load, the power dissipation is typically 10 nW per gate
 - Power consumption increases with higher clock speeds
- Short propagation delays (around 25 ns)
- Good noise immunity (50% or 45% of the full logic)
 - $NM_H = NM_L = 3(V_{DD} + 2V_{th}/3)/8$
- Levels of the logic signal will be equal to V_{DD} since the input impedance is so high.
- Voltage levels range from 0 to V_{DD}
- A low level is between 0 and $1/3 V_{DD}$ while a high level is between $2/3 V_{DD}$ and V_{DD}

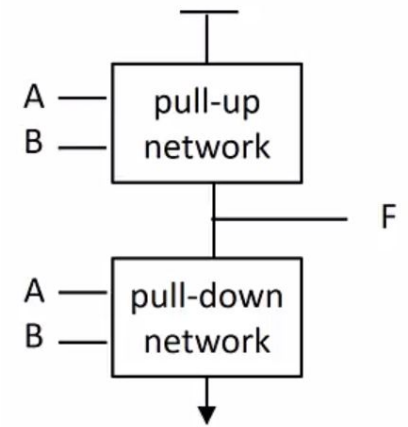






Pull-up: PMOS only
Pull-down: NMOS only

Fundamentals of Electronic Circuits (CMOS)

❖ Basic Logic Gates

❖ Useful links

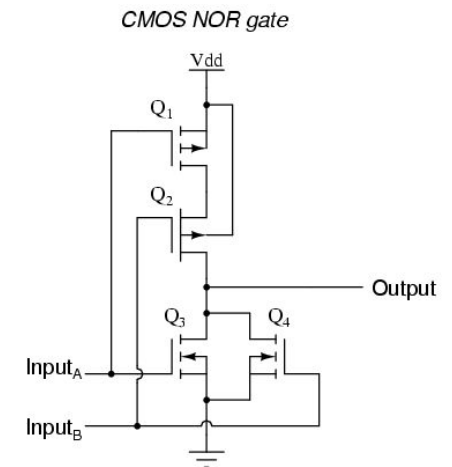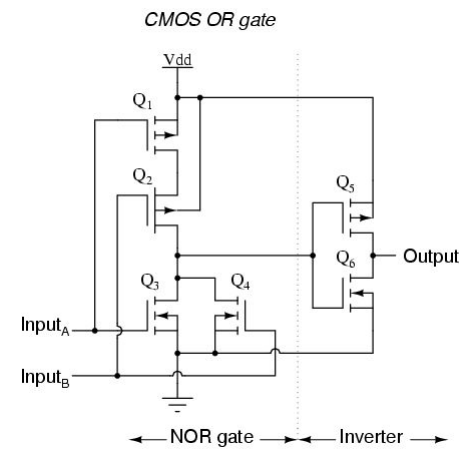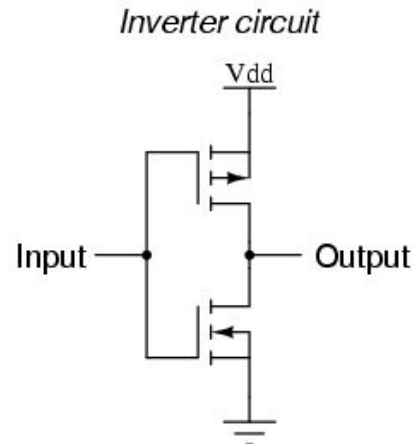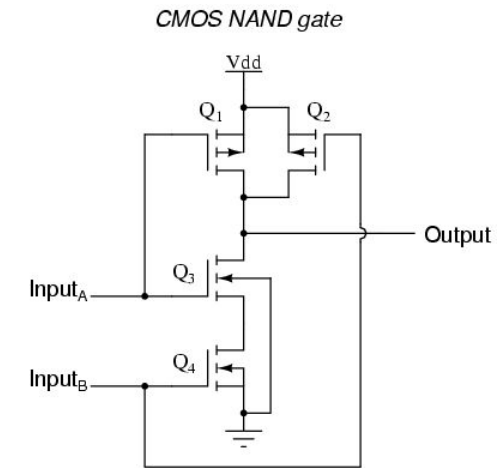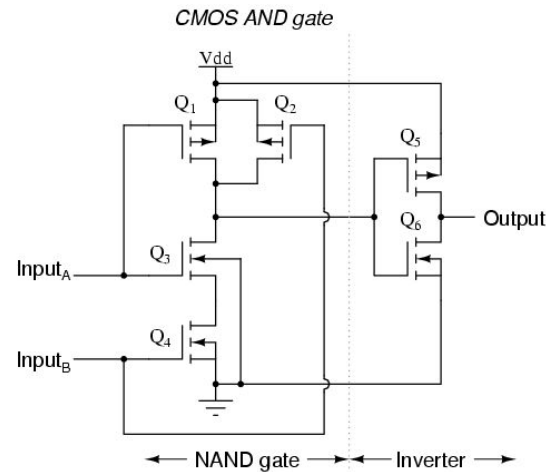- [CMOS Gate Circuitry](#)
- [CMOS Logic Gates](#)
- [CMOS Transistors](#)
- [CMOS Introduction](#)



Fundamentals of Electronic Circuits

❖ Some useful links

- [MOSFET BJT or IGBT - Brief comparison Basic components](#)
- [The FET \(field effect transistor\)](#)
- [How FETs Function - The Learning Circuit](#)
- [What is Field Effect Transistor - FET - JFET - MOSFET - Applications of MOSFET](#)
- The MOSFET ([part 1](#), [part 2](#) and [part 3](#))
- [MOSFET](#)
- [Field Effect Transistor \(FET\)](#)
- [Depletion MOSFETs](#)
- [Understanding The FinFet Semiconductor Process](#)
- [Investing in FinFET Technology Leadership Presented by ARM](#)
- [Samsung Foundry's New Transistor Structure](#)
- [Using Power MOSFETS with Arduino](#)